
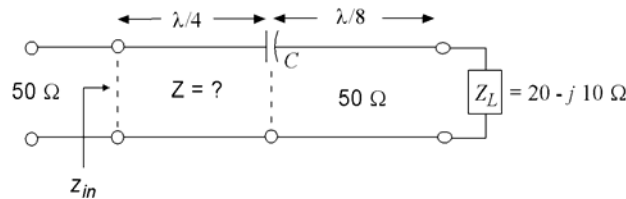


**Reading Assignment:** Cheng Chapter 10 & Handouts**Homework #6****Due: Friday 3 March 2006**

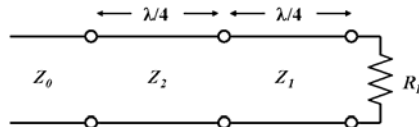- 1) Do problem P.9-26 in Cheng
- 2) A parallel RC load with  $R = 100\Omega$  and  $C = 1.5\text{ pF}$  is to be matched to a  $50\Omega$  line over a frequency band from 2 to 10GHz. What is the best return loss over this band that can be obtained with an optimum matching network?
- 3) Consider the problem below where a load  $Z_L = 20 - j10\Omega$  at 10GHz terminates a  $50\Omega$  transmission line. You are asked to design a matching network at this frequency, but due to physical constraints you can not use stubs. You have at your disposal only a chip capacitor  $C$ , and an ability to adjust the characteristic impedance of the main line if necessary.



- a) Find the required capacitance  $C$  such that when inserted in series at a distance  $\lambda/8$  from the load, the resulting input impedance is real. You may use a Smith chart but it is not required.
  - b) Then determine the necessary characteristic impedance of a quarter-wave transformer to provide a match to a  $50\Omega$  generator.
  - c) Would this procedure work for any arbitrary load impedance?
- 4) The equivalent circuit for the gate-source junction of a GaAs FET device is usually well modelled by a series  $RC$  circuit. Using a Smith chart, design a single-stub input matching network for a FET with  $R = 5\Omega$  and  $C = 0.2\text{ pF}$ , assuming a center frequency of  $f = 10\text{ GHz}$ . (Note: I've exaggerated the magnitude of  $R$  to make the problem slightly easier;  $R$  is more typically 1-2 Ohms or less). Then, using ADS, plot the frequency response of your design over a range of frequencies in the neighborhood of 10 GHz. What is the 3 dB bandwidth of your design?
  - 5) The bandwidth of a quarter-wave matching networks is determined by the load-source impedance transformation ratio,  $R_L/Z_0$ . The bandwidth can be improved by using several cascaded quarter-wave sections to gradually transform the impedance, such that each section in the cascade operates at a transformation ratio closer to unity as compared to a single quarter-wave section.



Find the characteristic impedances  $Z_1$  and  $Z_2$  of the 2-section impedance transformer above that will optimize the bandwidth. Simulate this structure on ADS using  $R_L = 200\Omega$  and  $Z_0 = 50\Omega$ , and compare with the response of a single-section quarter-wave transformer.