

# Temperature Dependence

Start with diode *I-V* relation:

$$I = I_s \left[ e^{qV_d/nkT} - 1 \right] \approx I_s e^{V_d/nV_T} \quad \Rightarrow \quad V_d \approx nV_T \ln \frac{I}{I_s} \quad V_T = \frac{kT}{q}$$

**Note:**  $I_s \propto T^3 e^{-E_g/kT}$


$E_g$  = bandgap energy = 1.13 eV (Si)

$$\frac{\partial I_s}{\partial T} \approx \frac{I_s}{T} \left( 3 + \frac{E_g}{kT} \right)$$

$k$  = Boltzman constant =  $8.62 \times 10^{-5}$  eV/°K

$q = 1.6 \times 10^{-19}$  C

For constant-current biasing:

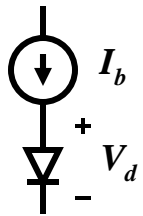

$$\text{TCV} = \frac{\partial V_d}{\partial T} \approx \frac{V_d}{T} - n \frac{V_T}{T} \left( 3 + \frac{E_g}{kT} \right)$$


$$T = 290 \text{ K}$$

$$I_d = 10 \text{ mA}$$

$$I_s = 1 \text{ pA}$$

$$n = 1$$
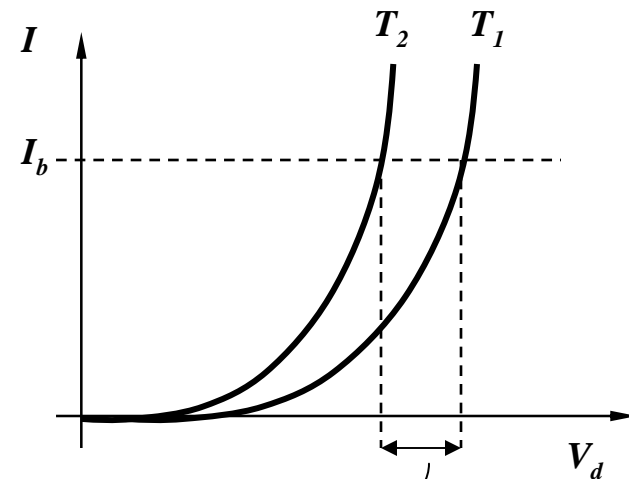
$$\text{TCV} \approx -2 \text{ mV/}^\circ\text{C}$$



$$\Delta V \approx -2 \text{ mV} (T_2 - T_1)$$


# Temperature Dependence

Note: for discrete diodes the ideality factor is closer to  $n=2$

*Significantly increased temperature coefficient*

Ex: 1N4005 measured data
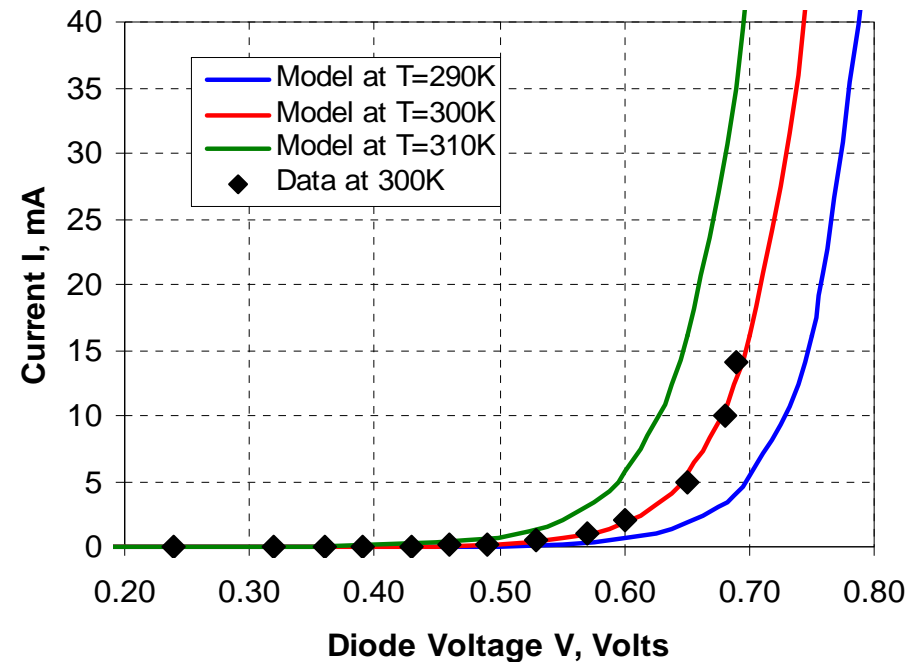
$$\left. \begin{array}{l} T = 300\text{K} \\ I_d = 10\text{mA} \\ I_s = 5.5\text{nA} \\ n = 1.82 \end{array} \right\} \text{TCV} \approx -5\text{mV}/^\circ\text{C}$$




The change in voltage or current in diodes and transistors must be dealt with in the design of circuits

Can be exploited too: a temperature sensor!
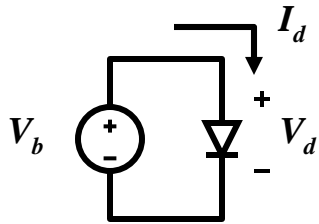
# Temperature Dependence


For constant-voltage biasing:  $I_d \approx I_s e^{V_b/nV_T}$



$$\text{TCI} = \frac{\partial I_d}{\partial T} \approx \frac{I}{T} \left( 3 + \frac{E_g}{kT} - \frac{qV_b}{nkT} \right)$$

$T = 300 \text{ K}$   
 $V_b = 0.65 \text{ V}$   
 $I_s = 1 \text{ pA}$   
 $n = 1$

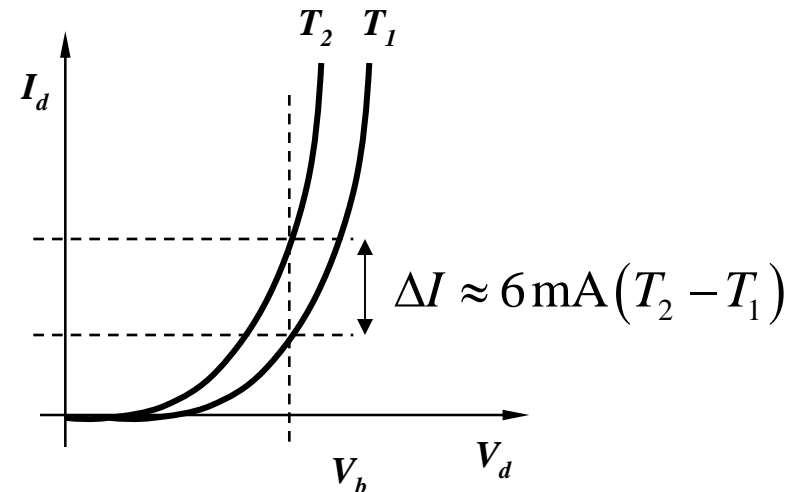
$I_d \approx 80 \text{ mA}$   
 $\text{TCI} \approx +6 \text{ mA}/^\circ\text{C}$



**Note: TCI depends exponentially on voltage and also a strong nonlinear function of temperature**

# Temperature Stabilization

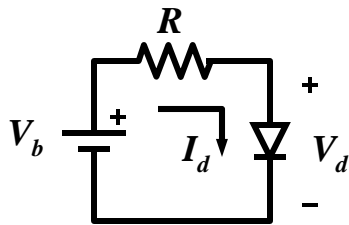**Biasing with a resistor and voltage source improves the stability with respect to temperature:**




$$V_d = V_b - R I_d$$

$$\frac{\partial V_d}{\partial T} = -R \frac{\partial I_d}{\partial T}$$

$$\frac{\partial I_d}{\partial T} = \frac{\text{TCI}}{\left(1 + \frac{R I_d}{n V_T}\right)}$$
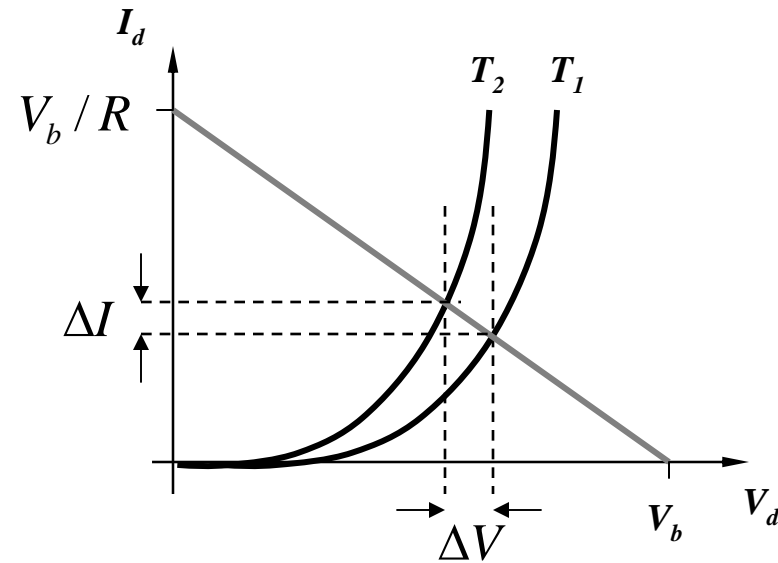
$$\frac{\partial V_d}{\partial T} = \frac{\text{TCV}}{\left(1 + \frac{n V_T}{R I_d}\right)}$$



**Usually:**  $R I_d \gg n V_T$

**So resistor biasing stabilizes current but voltage drift remains unchanged**