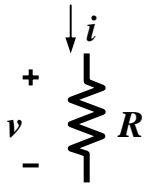



## Time Domain

## s-Domain



$$v = iR$$

$$V(s) = I(s)R$$

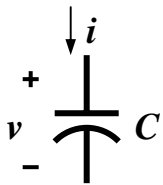


$$i = C \frac{dv}{dt}$$

$$I(s) = sCV(s) - Cv(0^-)$$

$$v(t) = \frac{1}{C} \int_0^t i dt + v(0^-)$$
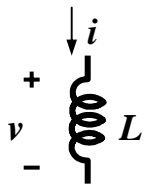
$$V(s) = \frac{1}{sC} I(s) + \frac{v(0^-)}{s}$$



$$v = L \frac{di}{dt}$$


$$V(s) = sLI(s) - Li(0^-)$$

$$i(t) = \frac{1}{L} \int_0^t v dt + i(0^-)$$


$$I(s) = \frac{1}{sL} V(s) + \frac{i(0^-)}{s}$$

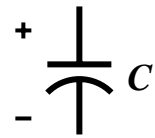
**Note initial conditions!**

Using the results of the previous slide we can draw equivalent s-domain circuits for capacitors and inductors to account for initial conditions:



→

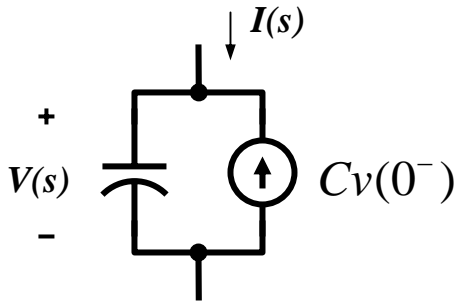

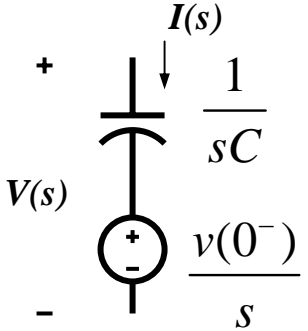


**Capacitor has an impedance:**  $\frac{1}{sC}$


$$I(s) = sCV(s) - Cv(0^-)$$


$$V(s) = \frac{1}{sC}I(s) + \frac{v(0^-)}{s}$$

Note polarity of sources!

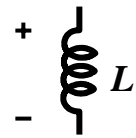

→

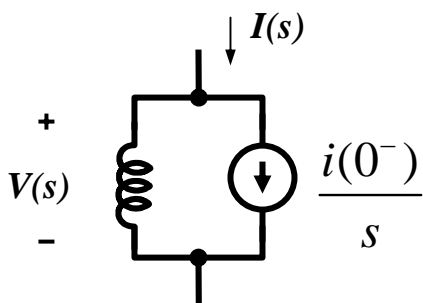

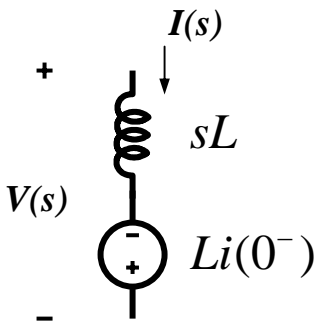

**Inductor has an impedance:**  $sL$

$$I(s) = \frac{1}{sL}V(s) + \frac{i(0^-)}{s}$$

$$V(s) = sLI(s) - Li(0^-)$$