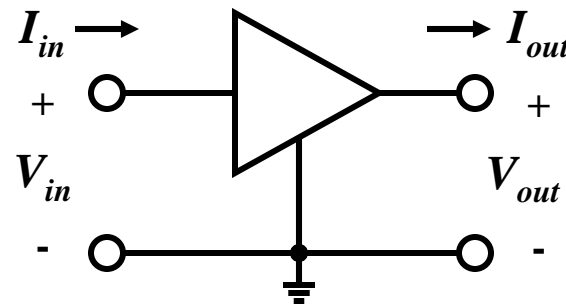



- An amplifier is a two-port device that takes a small input signal and generates a proportionally larger output signal
- The amplifier is “linear” if the output depends linearly on the input, e.g. $V_{out} = A_v V_{in}$
- Real amplifiers use nonlinear devices and hence can only approximate this behavior



- Amplifiers may respond to the input *voltage* or input *current* depending on the amplifying device used (eg. FET, BJT, tube) and the circuit
- Choice of equivalent two-port model depends on the type of amplifier

Impact of Input/Output Impedance

Voltage Amplifier

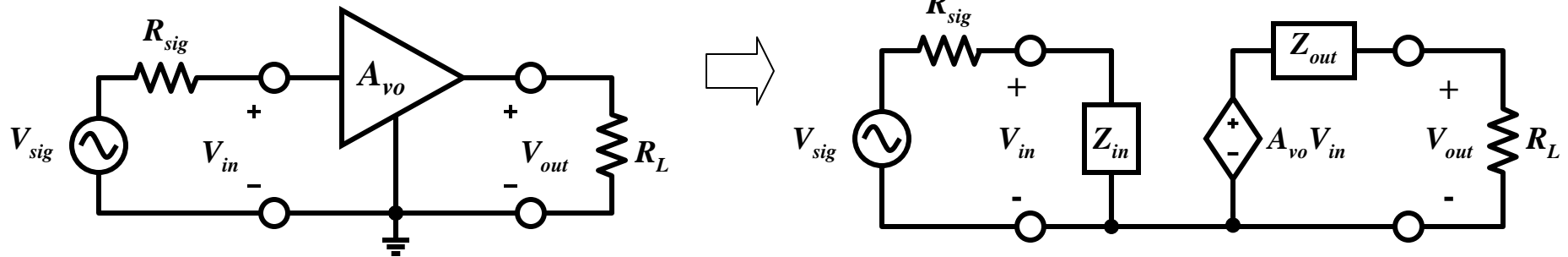

$$V_{in} = V_{sig} \left(\frac{R_{in}}{R_{in} + R_{sig}} \right) \quad V_{out} = A_{vo} V_{in} \left(\frac{R_L}{R_{out} + R_L} \right)$$

R_{in} forms a voltage divider with R_{sig}
 R_{out} forms a voltage divider with R_L

$$V_{out} = A_{vo} V_{sig} \left(\frac{R_{in}}{R_{in} + R_{sig}} \right) \left(\frac{R_L}{R_{out} + R_L} \right)$$

Note that if


$$\left. \begin{array}{l} R_{in} \gg R_{sig} \\ R_{out} \ll R_L \end{array} \right\} V_{out} \Rightarrow A_{vo} V_{sig}$$

So a voltage amplifier will work best under arbitrary source and load conditions if:

$$R_{in} \rightarrow \infty \quad R_{out} \rightarrow 0$$


Amplifier Equivalent Circuits

Voltage Amplifier

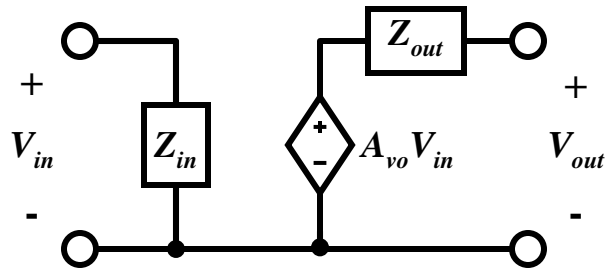


Ideal: $Z_{in} \rightarrow \infty$, $Z_{out} \rightarrow 0$

Current Amplifier

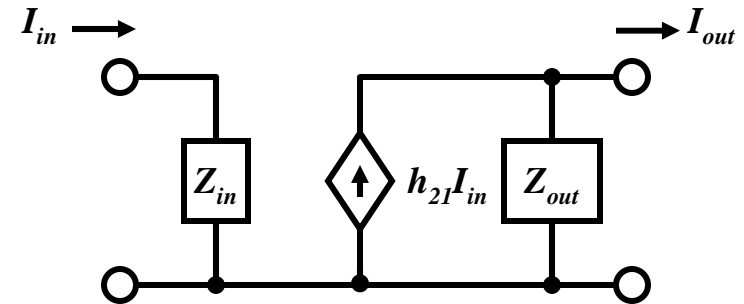


Ideal: $Z_{in} \rightarrow 0$, $Z_{out} \rightarrow \infty$

Trans-Impedance Amplifier

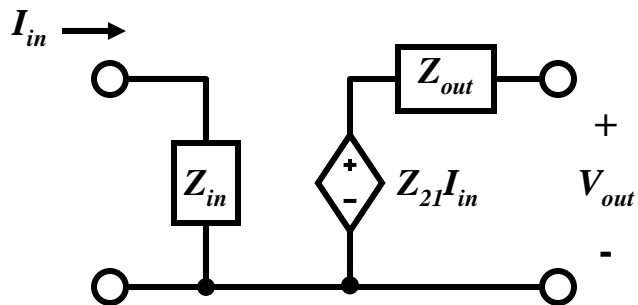

Ideal: $Z_{in} \rightarrow 0$, $Z_{out} \rightarrow 0$

Trans-Conductance Amplifier

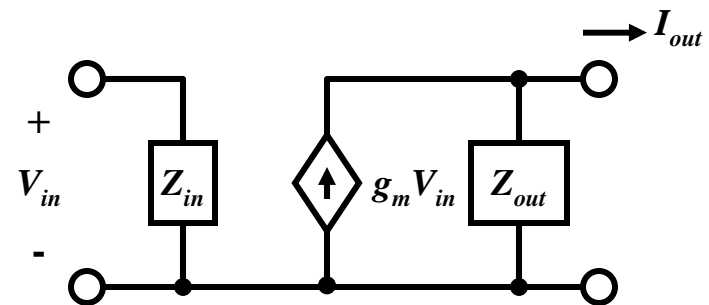

Ideal: $Z_{in} \rightarrow \infty$, $Z_{out} \rightarrow \infty$