


$$V_1 = L_1 \frac{dI_1}{dt} \pm L_m \frac{dI_2}{dt}$$

$$V_2 = \pm L_m \frac{dI_1}{dt} + L_2 \frac{dI_2}{dt}$$

- Correct sign for mutual inductance found from Lenz' law and dot convention
- Dot convention: current flowing *into* one dot will induce current flow *out* of second dot

A transformer is just a special case where the mutual inductance is made as large as possible by allowing both coils to share the same flux

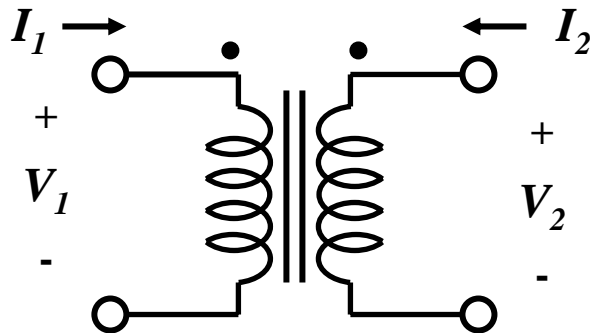This is usually achieved by winding them both on a common core of high permeability material (soft iron or ferrite materials)



$$V_1 = j\omega L_1 I_1 + j\omega L_m I_2$$


$$V_2 = j\omega L_m I_1 + j\omega L_2 I_2$$

When there is no flux leakage, the mutual inductance is related to the primary and secondary inductances as

$$L_m = \sqrt{L_1 L_2}$$

For real transformers this can never be quite achieved, so we write
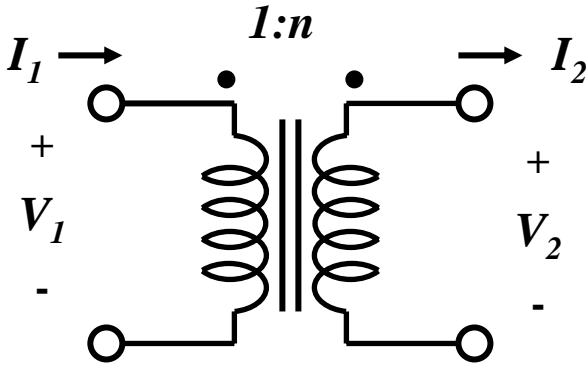
$$L_m = k \sqrt{L_1 L_2} \quad \text{where} \quad 0 < k < 1 \quad \text{coefficient of coupling}$$



If both coils share the same flux, then Farady's law gives:


$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{1}{n}$$

As the permeability of the core increases, the relationship between the primary and secondary currents approaches a limiting value set by the turns ratio:

$$\frac{I_1}{I_2} \Rightarrow \frac{N_2}{N_1} = n$$


These two relationships define an *ideal transformer*. This is a fictitious element (note that  $\mu \rightarrow \infty$  implies infinite inductances so the impedance matrix is infinite) but a real transformer approaches this behavior.

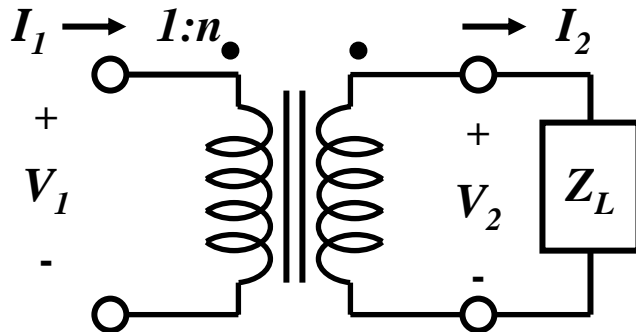An idea transformer has the following property when one winding is terminated:



$$Z_{in} = \frac{V_1}{I_1} = \frac{(N_1 / N_2)V_2}{(N_2 / N_1)I_2} = \frac{Z_L}{n^2}$$

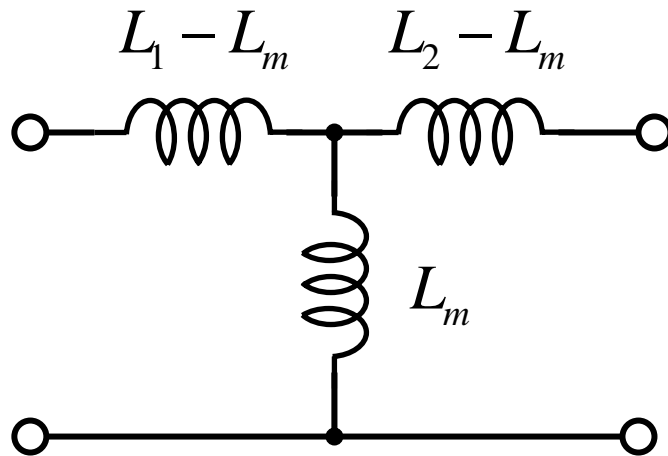Using the tee-equivalent for reciprocal networks, we find the following equivalent circuit for mutual inductances or transformers




$$L_1 \propto N_1^2$$

$$L_2 \propto N_2^2 = n^2 L_1$$

$$L_m = k \sqrt{L_1 L_2} = kn L_1$$

This can be cascaded with an ideal 1:1 transformer to simulate the fact that a real transformer has electrically isolated ports

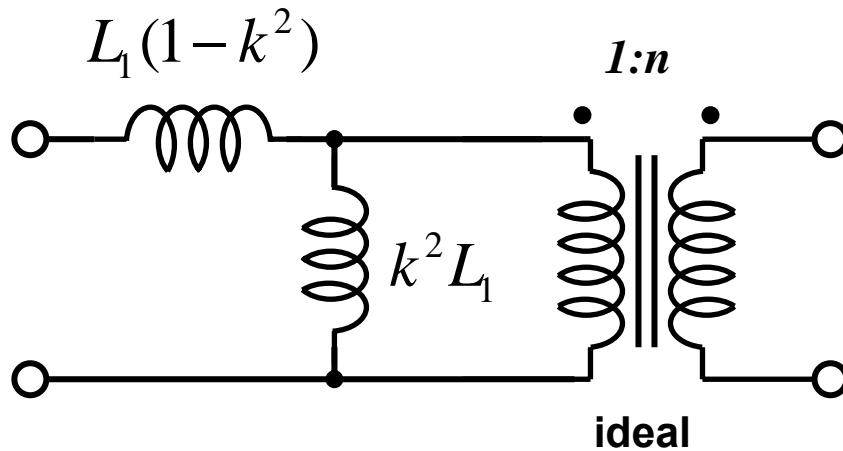The following is also an identical equivalent that uses an ideal transformer to explicitly incorporate the turns ratio and isolation between ports



$$n = \frac{L_2}{L_m}$$

For good transformers,  $k$  is nearly 1, and this model shows why real transformers do not work at DC